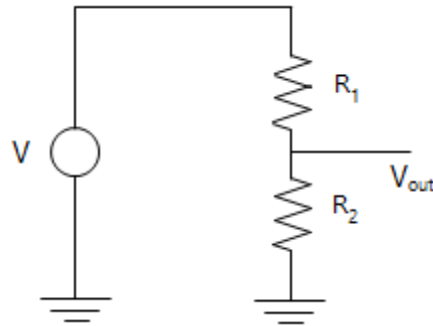


Extreme Value Analysis of a Voltage Divider

This application performs an extreme value analysis of a voltage circuit.



Parameter Values

Number of components

$$N := 3$$

Nominal values for V , R_1 and R_2

$$\text{nom} := \begin{bmatrix} 5 \text{ V} \\ 86.7 \text{ k} \\ 11 \text{ k} \end{bmatrix}$$

Upper and lower % tolerances for V , R_1 and R_2

$$\text{upper_tol} := \begin{bmatrix} 0.1 \\ 0.05 \\ 0.01 \end{bmatrix} \quad \text{lower_tol} := \begin{bmatrix} 0.1 \\ 0.05 \\ 0.01 \end{bmatrix}$$

Voltage equation

$$V_{\text{out}} := (V, R_1, R_2) \frac{V \cdot R_2}{R_1 + R_2}$$

Voltage at the nominal component values

$$V_{\text{out}}(\text{nom}[1], \text{nom}[2], \text{nom}[3]) = 0.563 \text{ V}$$

Extreme Value Analysis

Calculate every combination of tolerance values

```
zeta := Vector( 2^N, i subs( 0 = -1,
Bits:-Split( i, bits = N) ) )
```

$$zeta = \begin{bmatrix} [1, -1, -1] \\ [-1, 1, -1] \\ [1, 1, -1] \\ [-1, -1, 1] \\ [1, -1, 1] \\ [-1, 1, 1] \\ [1, 1, 1] \\ [-1, -1, -1] \end{bmatrix}$$

```
zeta2 := Vector( 2^N, i 1 + ~ zeta[i] · ~
[ seq( ifelse( zeta[i][j] = 1, upper_tol[j],
lower_tol[j] ), j = 1..N) ] )
```

$$zeta2 = \begin{bmatrix} [1.100, 0.950, 0.990] \\ [0.900, 1.050, 0.990] \\ [1.100, 1.050, 0.990] \\ [0.900, 0.950, 1.010] \\ [1.100, 0.950, 1.010] \\ [0.900, 1.050, 1.010] \\ [1.100, 1.050, 1.010] \\ [0.900, 0.950, 0.990] \end{bmatrix}$$

Calculate the voltage at every combination of extreme tolerance values

```
V := Vector( 2^N, i V_out( seq( nom[j] ·
zeta2[i][j], j = 1..N) ) )
```

$$V = \begin{bmatrix} 0.642 \text{ V} \\ 0.481 \text{ V} \\ 0.588 \text{ V} \\ 0.535 \text{ V} \\ 0.654 \text{ V} \\ 0.489 \text{ V} \\ 0.598 \text{ V} \\ 0.525 \text{ V} \end{bmatrix}$$

Extreme values of voltage

$$\min(V) = 0.481 \text{ V}$$

$$\max(V) = 0.654 \text{ V}$$